

a). Design a circuit to verify Kirchoff's Voltage law for input voltages $V=8V$. The circuit uses $R_1= 1k\Omega$ and $R_2= 2 k\Omega$. This setup is connected across a constant voltage source. Also, verify the results practical and theoretical values

a). Design an electrical circuit to verify Kirchoff's current law for three different input voltages which have two resistors $R_1= 560 \text{ ohm}$ and $R_2= 560 \text{ ohm}$ connected in parallel and this combination is connected across a constant DC source. Also, verify the results by current division rule.


a). Analyze the given circuit where a resistor $R_1=5 k\Omega$, $R_2=10k\Omega$, and $R_3=7.5 k\Omega$ are connected in a series circuit powered by a 15 V DC source

a). Analyze the given circuit where resistors $R_1=1k\Omega$, $R_2=3k\Omega$, and $R_3=2k\Omega$ are connected in parallel to a 6V DC source.


a). A 12V voltage source is connected in series with two resistors, $R_1=4 \Omega$ and $R_2=6 \Omega$. The load resistor $R_L=8 \Omega$ is connected across the terminals where Thevenin's equivalent is to be found. Verify the results theoretically and practically.

a). A 12V voltage source is connected in series with two resistors, $R_1=4 \Omega$ and $R_2=6 \Omega$. The load resistor $R_L=8 \Omega$ is connected across the terminals where Thevenin's equivalent is to be found. Verify the results theoretically and practically.

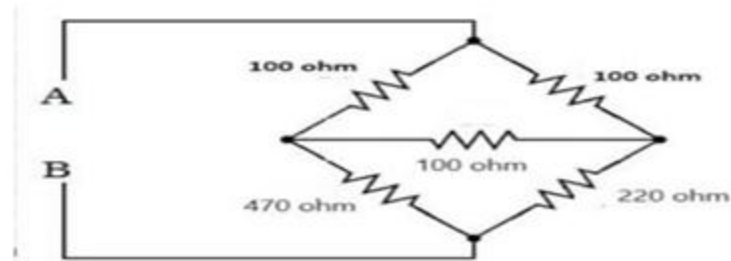
a). Design a circuit to verify star delta reduction technique for the bridge circuit shown below. Calculate the effective resistance between the terminals A & B theoretically and practically.



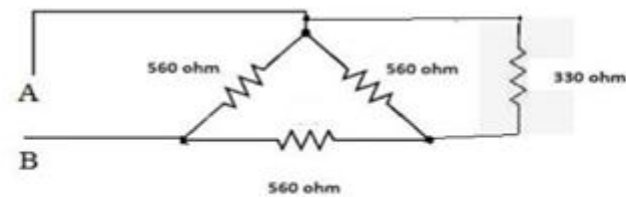
a). Design a circuit to verify star delta reduction technique for the circuit shown below. Calculate the effective resistance between the terminals A & B theoretically and practically



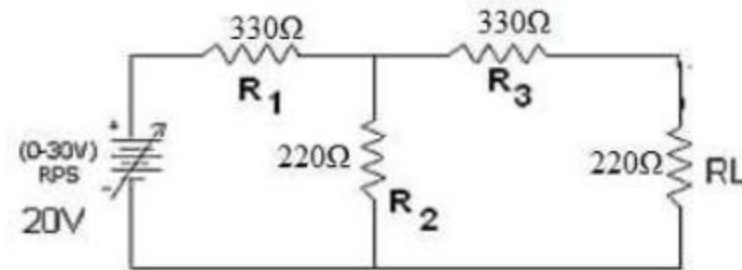
a). Determine the current flows through $330\ \Omega$ (R_3) resistor by applying Thevenin's & Norton's theorem theoretically and verify the results theoretically and practically. Assume 12V supply.



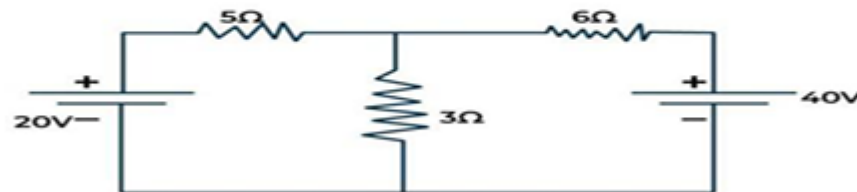a). Determine the current flows through $3\ \Omega$ resistor by applying Superposition theorem theoretically and verify the results theoretically and practically. Assume 20V supply.



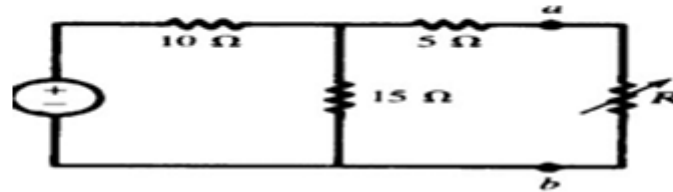- a). Find the value of the adjustable resistance R that dissipates the maximum power across terminals a-b. What is the maximum power that can be delivered to this load? Assume supply 15V.



- a) Design and determine the output characteristics of LVDT and calibrate the measuring instruments for given frequency and no of turns.

- a). Implement the domestic wiring used to control a single electrical load from two different places by using 2-way switches and a bulb. Also verify its operation using truth table.

S.NO	S1	S2	LAMP STATUS
1	CA	C'A'	ON
2	CB	C'B'	ON
3	CA	C'B'	OFF
4	CB	C'A'	OFF

